


APB SLAVE




Contents

- Block Diagram of Module
- Main Building Blocks of Module
- RTL
- Output waves

Block Diagram

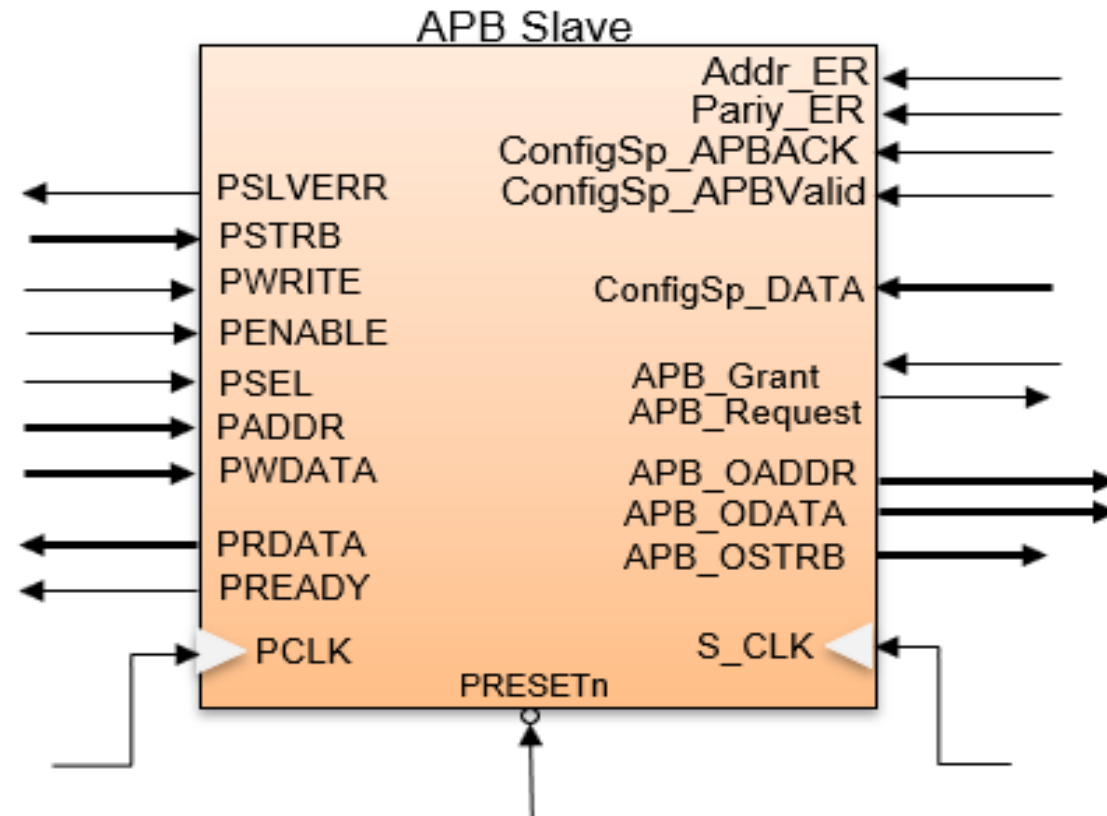


Main Building Blocks

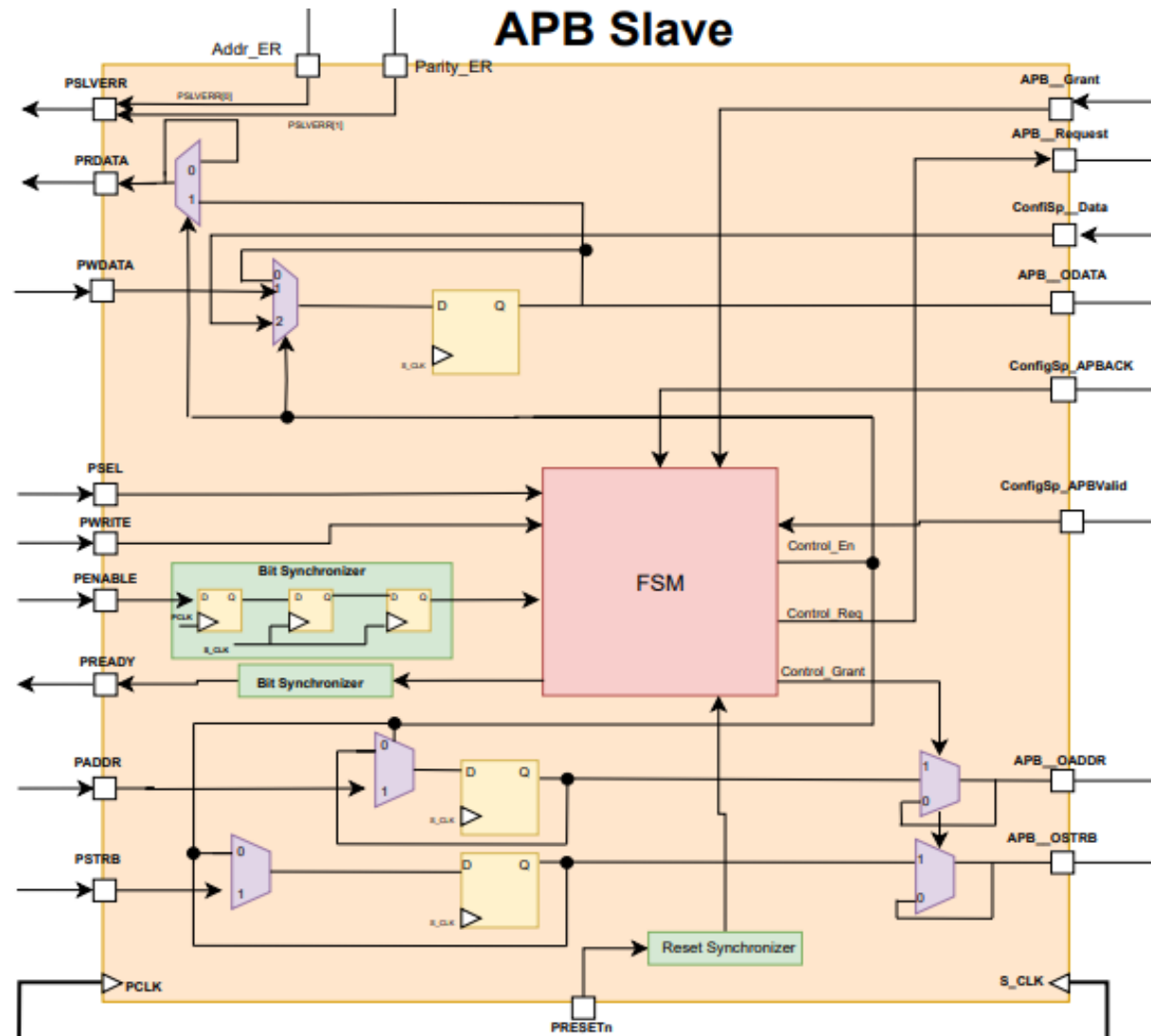

RTL : Bit Synchronizer with Pulse Converter

```
module BIT_SYNC (  
  input  wire  Destination_CLK,  
  input  wire  RST,  
  input  wire  ASYNC_IN,  
  output reg   SYNC_OUT  
);  
//Destination FlipFlop  
reg FF1;  
//Synchronization FlipFlop  
reg FF2;  
  
//flag  
reg Pulse_Conv_flg;  
  
//Sequential always  
always @(posedge Destination_CLK, negedge RST) begin  
  if(!RST) begin  
    FF1      <= 'b0;  
    FF2      <= 'b0;  
  end  
  else begin  
    FF1      <= ASYNC_IN;  
    FF2      <= FF1;  
  end  
end  
end
```

 

RTL : Bit Synchronizer with Pulse Converter

```
//Pulse Converter Logic
always@(posedge Destination_CLK, negedge RST) begin
    if(!RST) begin
        Pulse_Conv_flg      = 'b1;
    end

    else begin
        if(FF2 == 'b1) begin
            if(Pulse_Conv_flg == 'b1) begin
                SYNC_OUT      = 'b1;
                Pulse_Conv_flg = 'b0;
            end

            else begin
                SYNC_OUT      = 'b0;
                Pulse_Conv_flg = 'b0;
            end


        end

        else begin
            Pulse_Conv_flg      = 'b1;
            SYNC_OUT             = 'b0;
        end

    end



end

endmodule
```

 



RTL : Reset Synchronizer

- We have a problem with the Asynchronous reset de-assertion as it **may violate recovery time** which may get all the flip flops onto a **metastable state**.
- **$T_{Recovery}$** : it is the minimum time for sequential cells that the active low set or reset signal **must be de-asserted before the active edge** of the clock, to allow the circuit to be recovered from the effect of the asynchronous control signal and the next clock edge can trigger the circuit.

  

RTL : Reset Synchronizer

  - A reset synchronizer **synchronizes the de-assertion of reset** with respect to the clock domain.




RTL : Reset Synchronizer

```
module RESET_SYNC (  
    input    wire    Destination_CLK,  
    input    wire    RST,  
    output   reg     SYNC_RST  
);  
  
//Destination FlipFlop  
reg     FF1;  
  
//Sequential always  
always @(posedge Destination_CLK, negedge RST) begin  
    if(!RST) begin  
        FF1          <= 'b0;  
        SYNC_RST      <= 'b0;  
    end  
    else begin  
        FF1          <= 'b1;  
        SYNC_RST      <= FF1;  
    end  
end  
  
endmodule
```


Write Transaction : 1. Reset

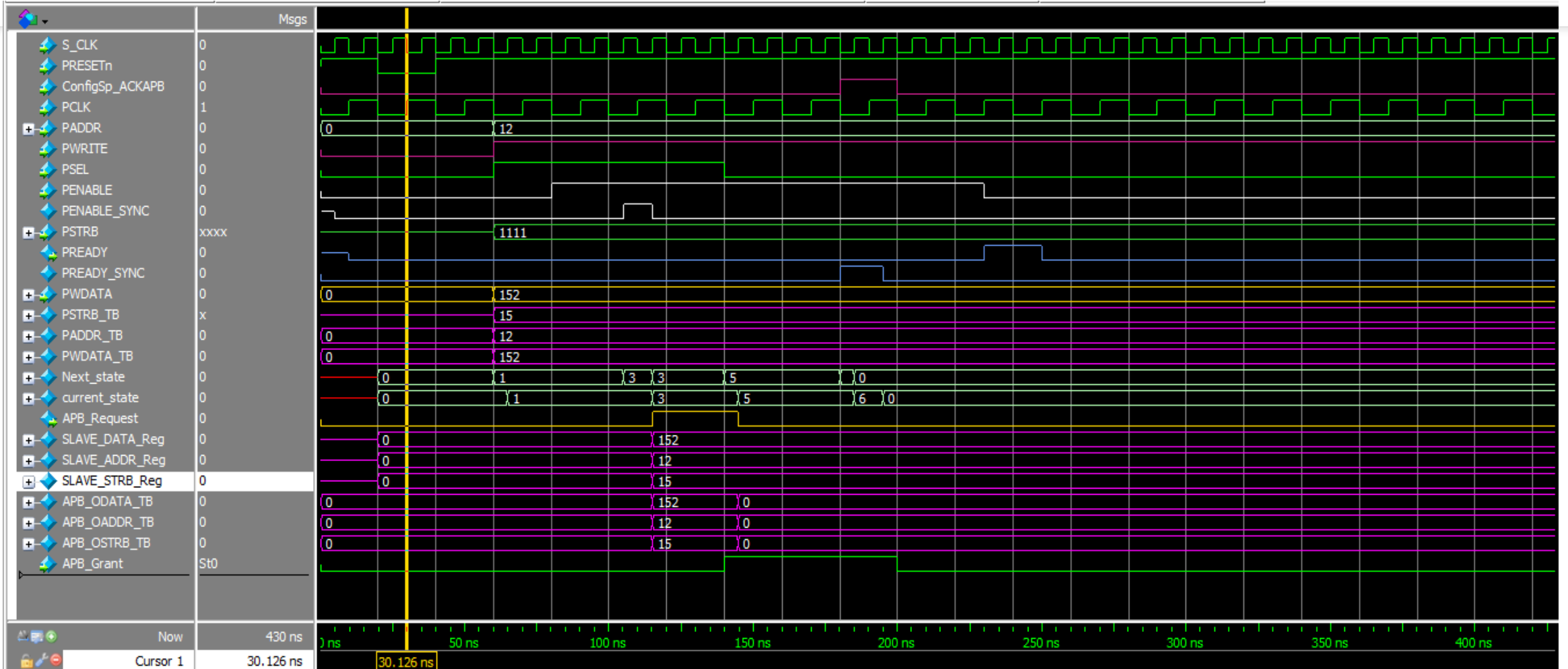(Data = 'd152, Address = d'12, Strobes = 'b1111)




Write Transaction : 2. Setup Phase

 (Data = 'd152, Address = d'12, Strobes = 'b1111)




Write Transaction : 3. Access Phase

 (Data = 'd152, Address = d'12, Strobes = 'b1111)




Write Transaction : 4. Storage Data on S_CLK

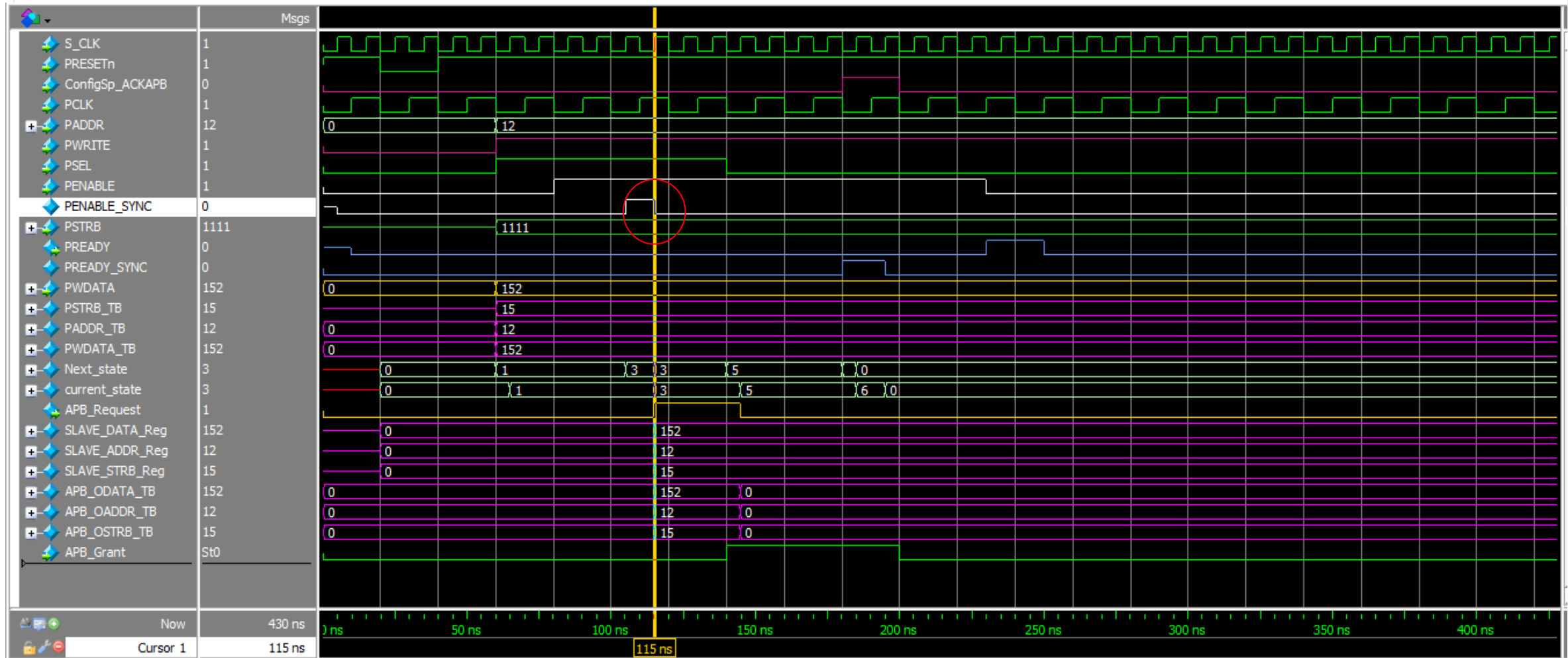(Data = 'd152, Address = d'12, Strobes = 'b1111)




Write Transaction : 5. Waiting for Grant Access

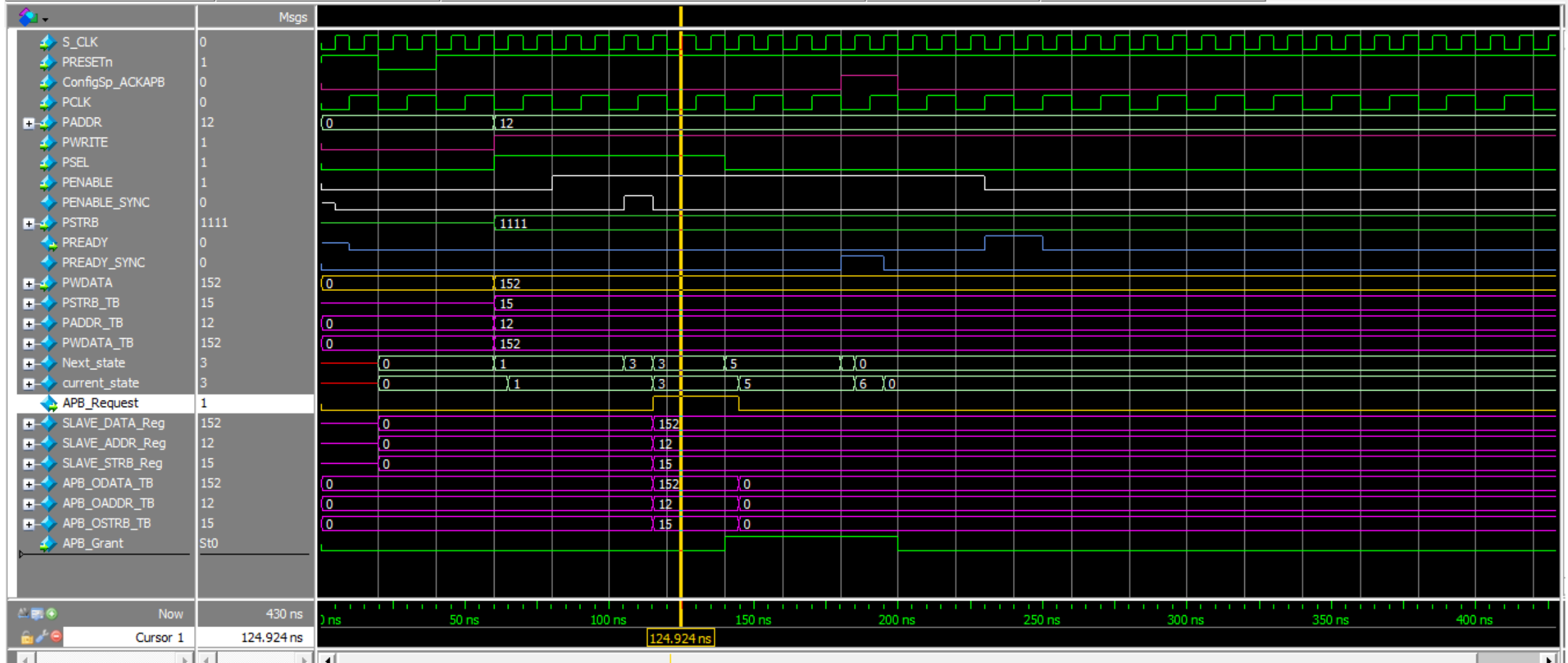(Data = 'd152, Address = d'12, Strobes = 'b1111)




Write Transaction : 6. Grant Access Approved

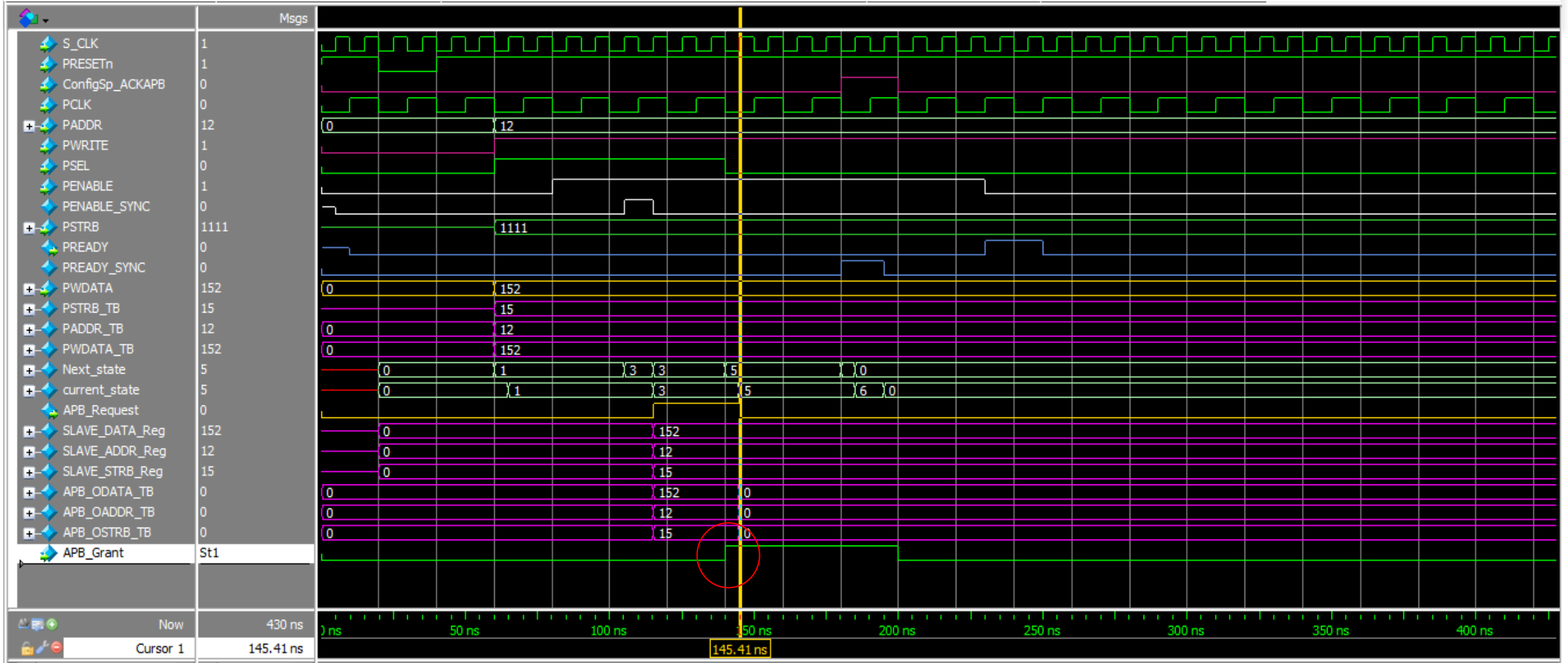(Data = 'd152, Address = d'12, Strobes = 'b1111)




Write Transaction : 7. Config Space ACK came

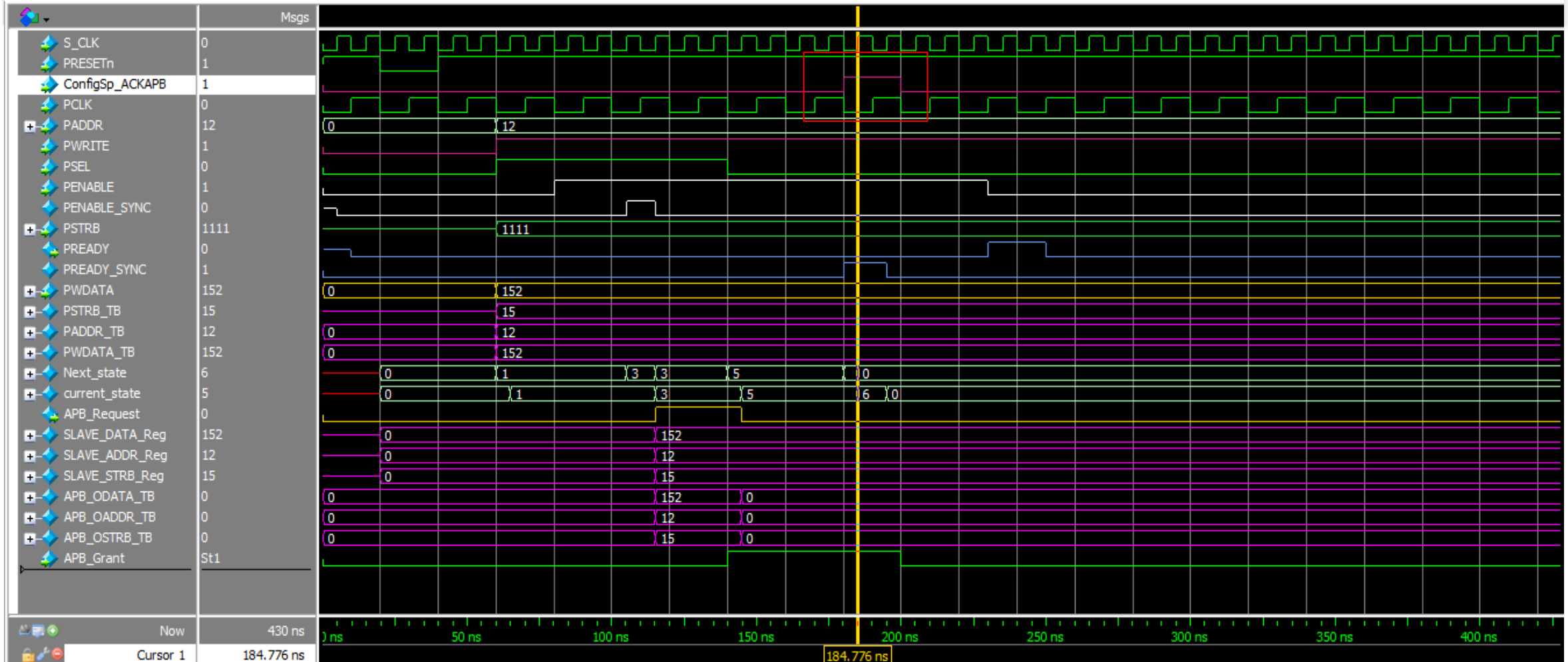(Data = 'd152, Address = d'12, Strobes = 'b1111)




❑ Write Transaction : 8. Transaction Completed
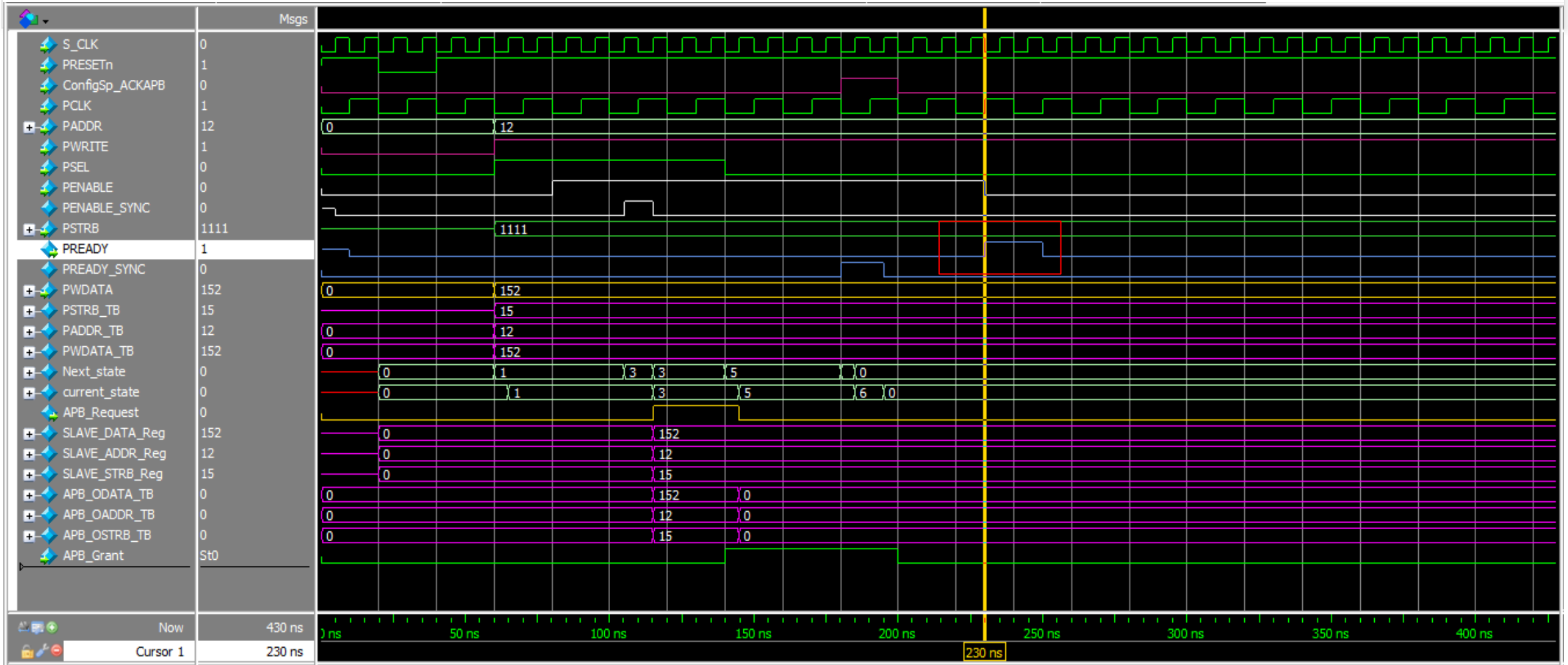
```
( Data = 'd152, Address = d'12, Strobes = 'b1111 )
```




Read Transaction : 7. CS ACK and Valid Came

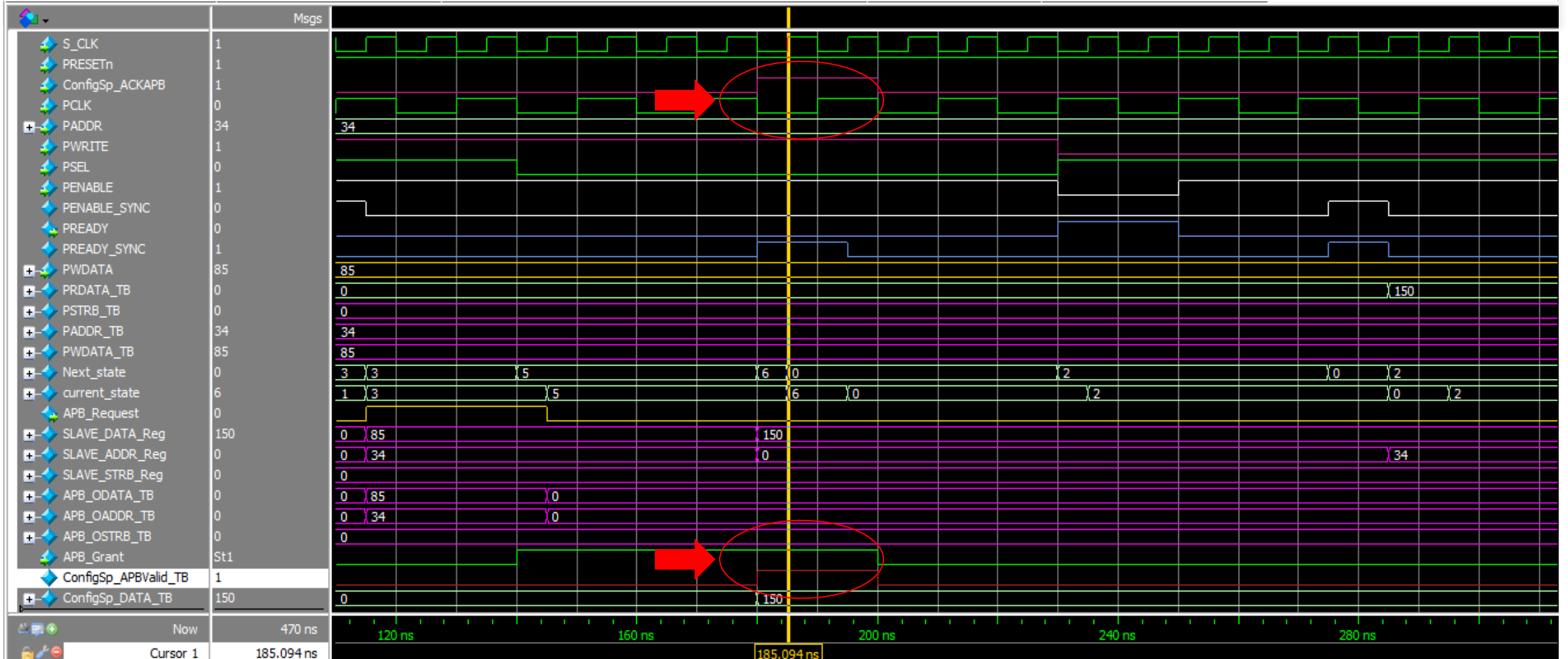(Data = 'd85, Config Space data = 'd150 Address = d'34, Strobes = 'b0000)



Read Transaction : 8. Reading CS Data ('d150)

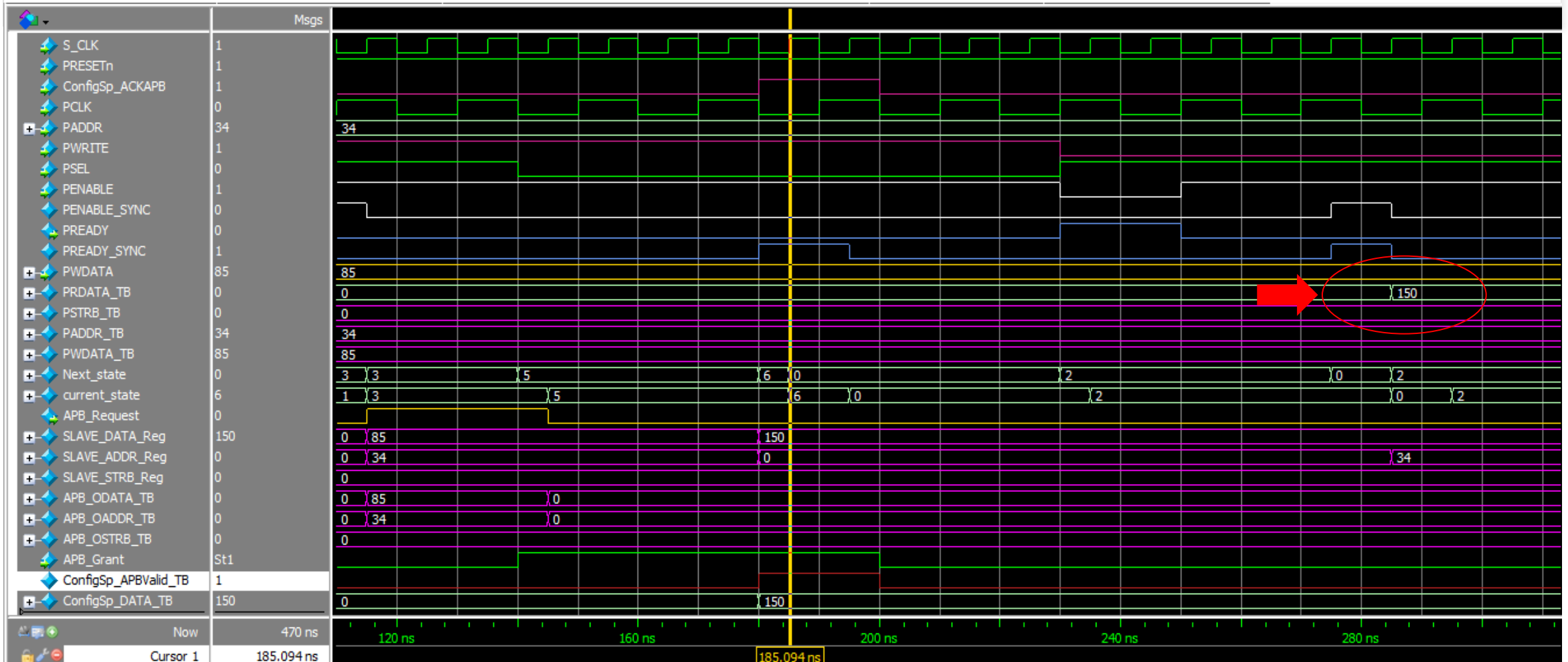(Data = 'd85, Config Space data = 'd150 Address = d'34, Strobes = 'b0000)





Any Questions ?